

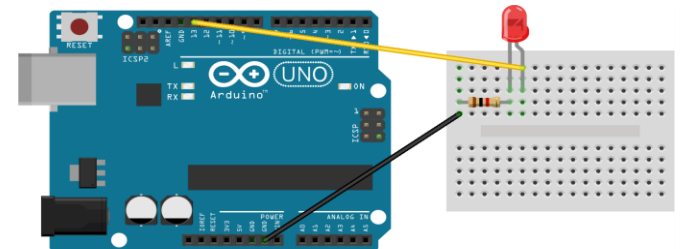


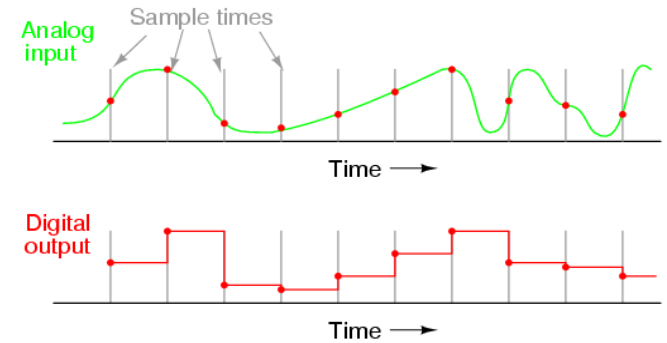

**MUFE**  
MARMARA UNIVERSITY - FACULTY OF ENGINEERING  
**ROBOTICS TEAM**

# Neler gördük?

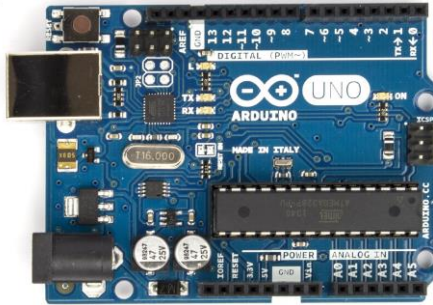


Made with Fritzing.org

# Elektrik – Elektroniğe Giriş

## Robot Enerji Kaynağı

# Li-Po Pil

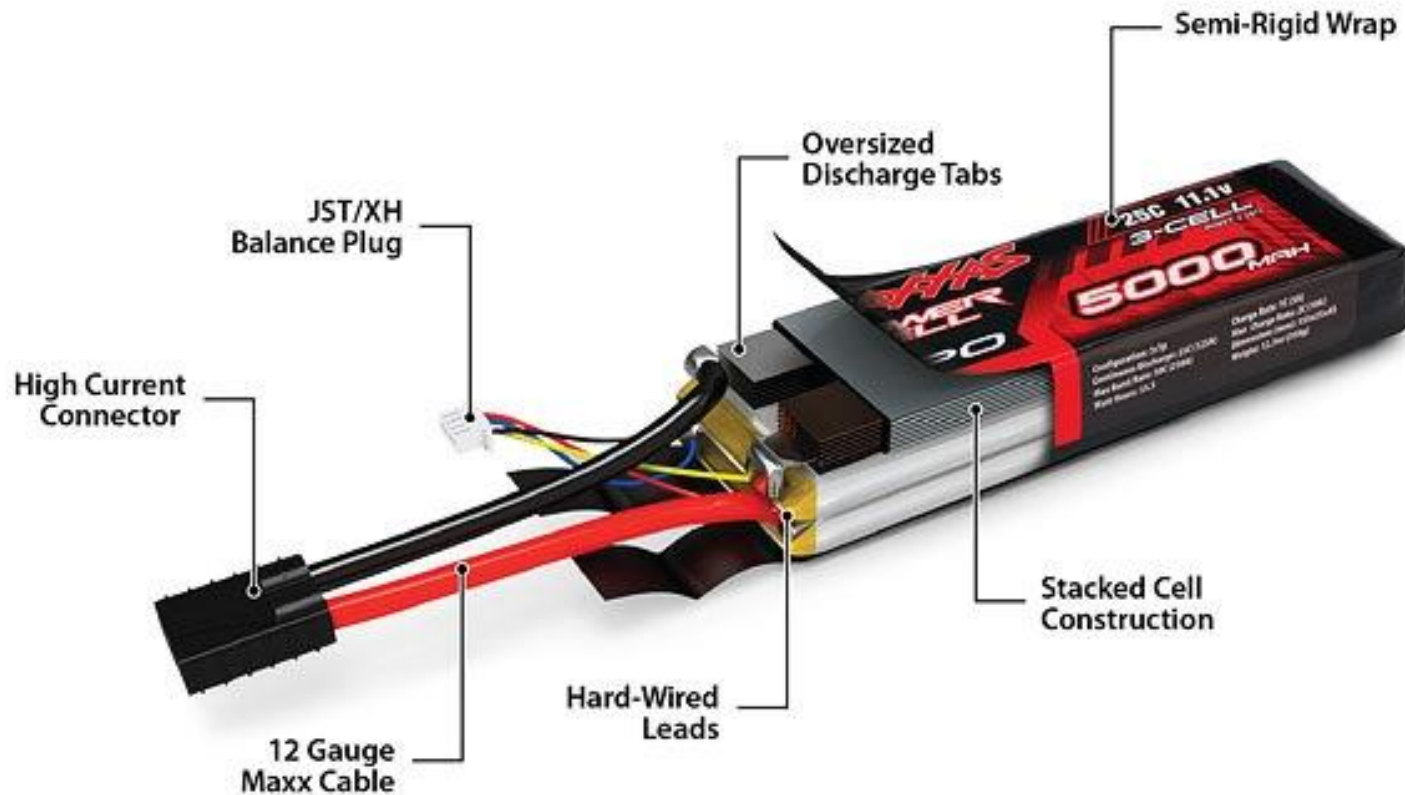

# Otonom Robotlar

- Algılama
- Hareket
- Enerji
- Zeka



# Pil Voltajları



Li-Po 2S 7,4Volt  
1000mAh



Li-Po 3S 11,1Volt  
2200mAh



Li-Po 4S 14,8Volt  
1300mAh

# Genel Çalışma Voltajları



5,0 Volt



3,3 - 5,0 Volt



3,0 - 12,0 Volt



10,0 Volt



6,0 – 7,2 Volt



5,0 – 15,0 Volt  
(Regülatör)





5,0 Volt

**Sorularınız?**



# Elektrik – Elektronik Giriş Sinyal

# Digital – Analog Sinyaller

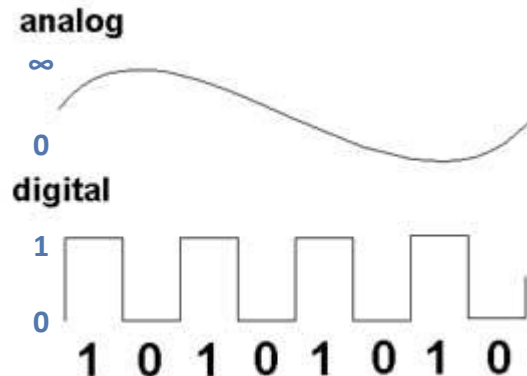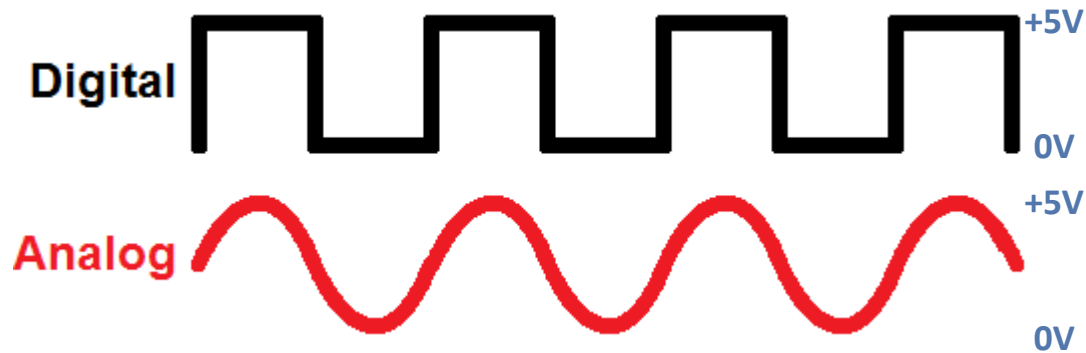


**MÜHENDİSLİK FAKÜLTESİ ROBOT TAKIMI – MUFE ROBOTICS**




## 1 = HIGH = +5 Volt = Yes Voltage

# Digital Sinyal İle Çalışanlar

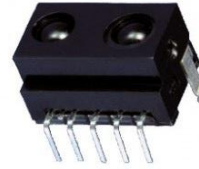

# Analog Input

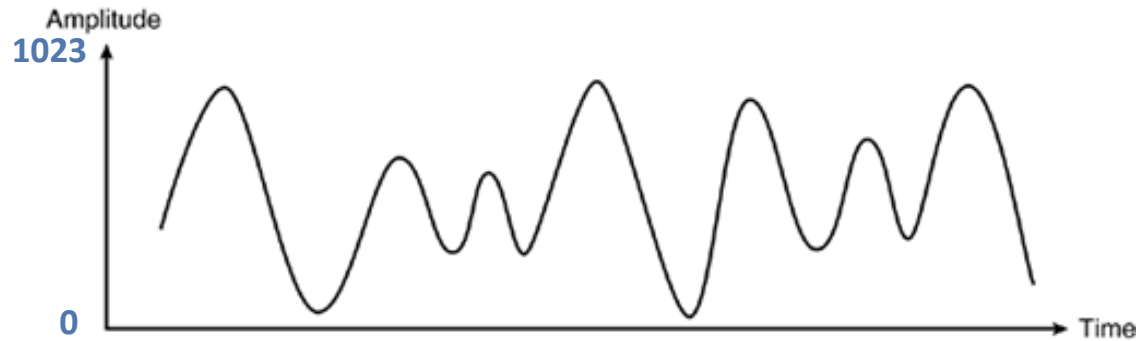


**0 = 0 Volt = Low Voltage**

**1023 = +5 Volt\* = High Voltage**

\*Maximum Analog voltajı kullanılan sisteme ve referans voltajına göre farklılık gösterebilir.

# Analog Output (PWM)

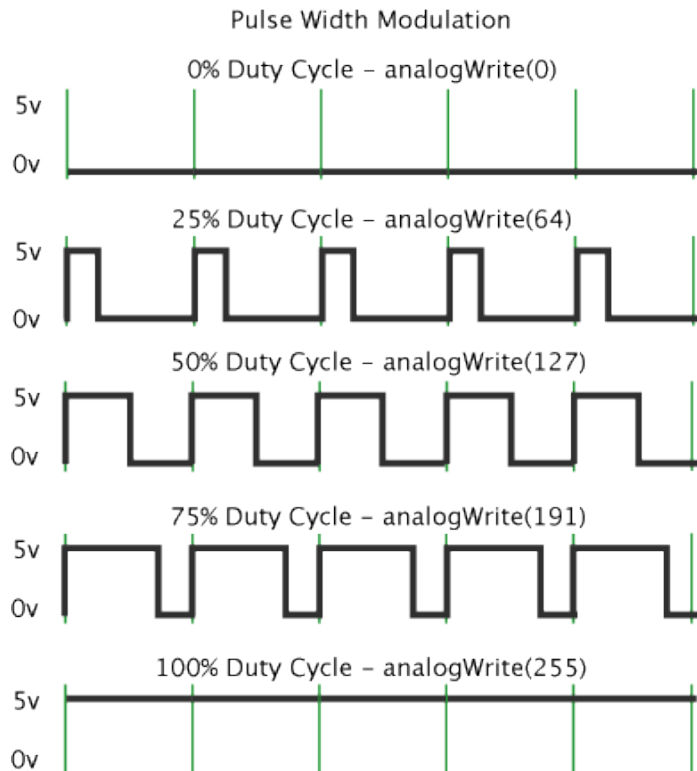

**0 = 0 Volt = No Voltage**

**64 = ~1,25 Volt**

**127 = ~2,5 Volt**

**191 = ~3,75 Volt**

**255 = +5 Volt = High Voltage**

# Analog Sinyal İle Çalışanlar




**Sorularınız?**



# Elektrik – Elektroniğe Giriş



## Devre Elemanları

# Elektrik - Elektronik

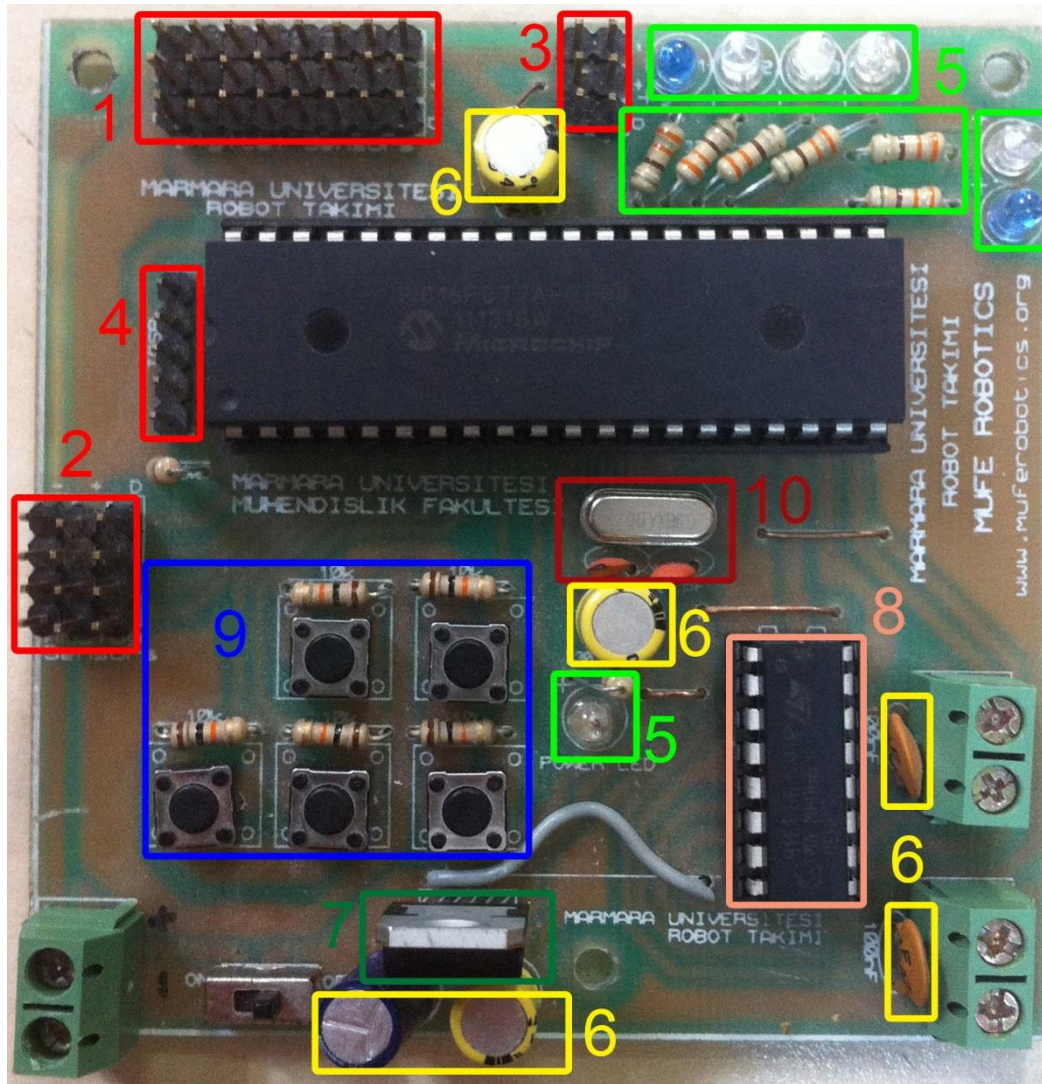

- 1- Digital I/O PINS PORT B
- 2- Analog I/O PINS PORT A
- 3- Digital I/O PINS PORT D
- 4- ICSP Program PINS
- 5- LED Devreleri
- 6- Capacitors (Ceramic / Electrolytic)
- 7- LM7805 – 5V Regulator
- 8- L293D – Motor Driver
- 9- Button Devreleri
- 10- Crystal Oscillator Devresi



# Button

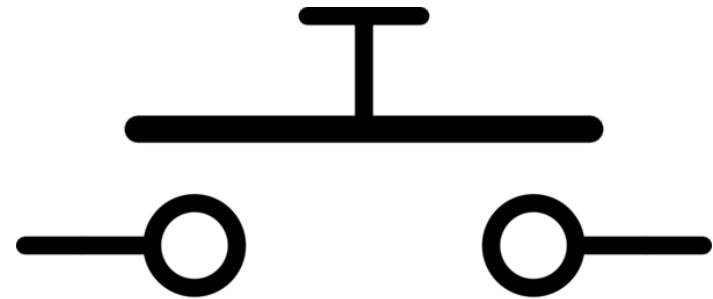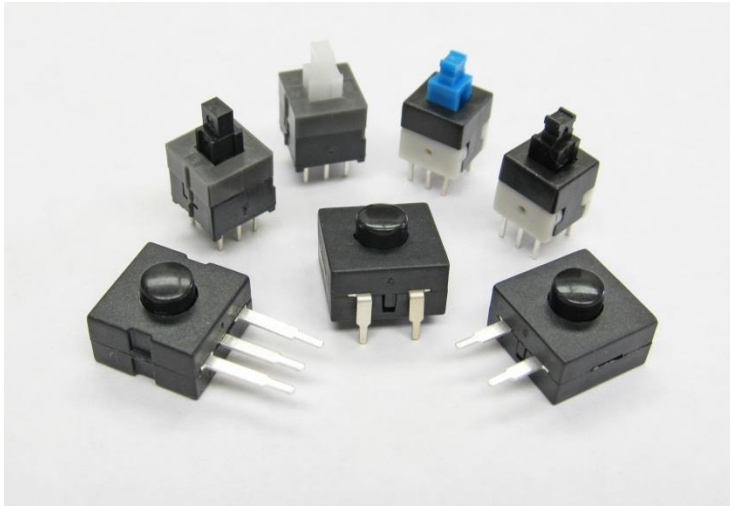


**SW1**



# Switch


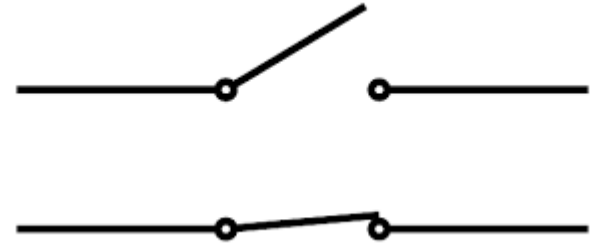
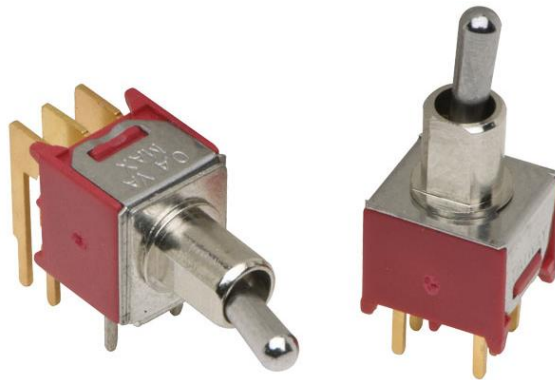


## LED

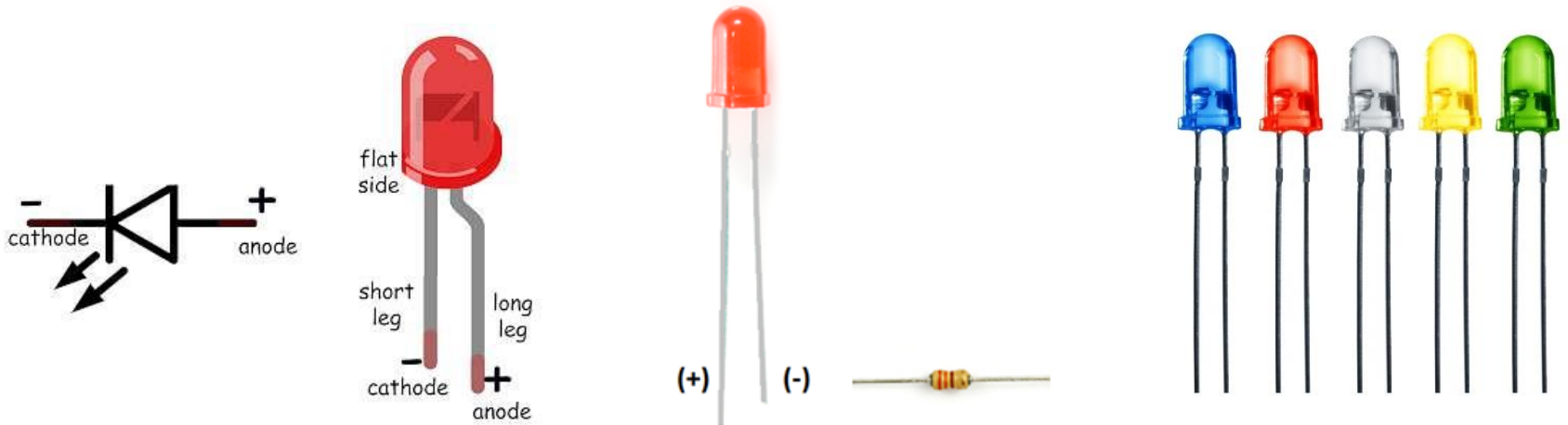


## 5mm LED (Light Emitting Diode)


## Direnç

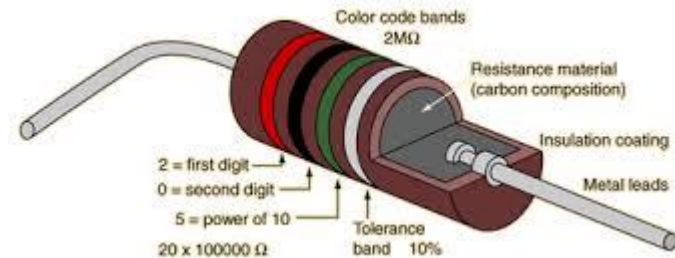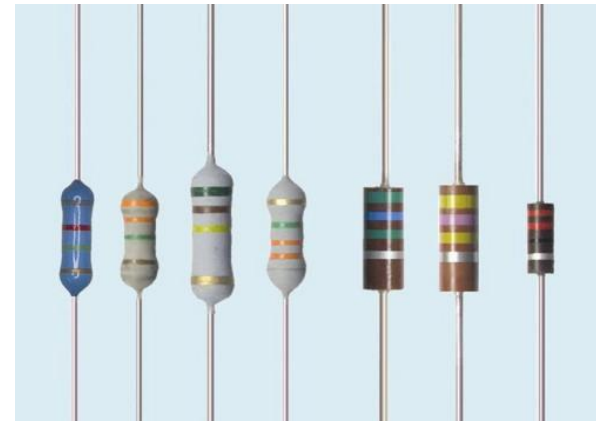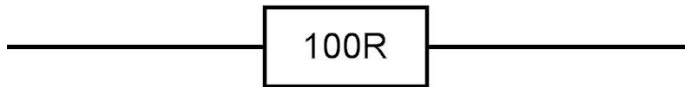

# LED Devresi


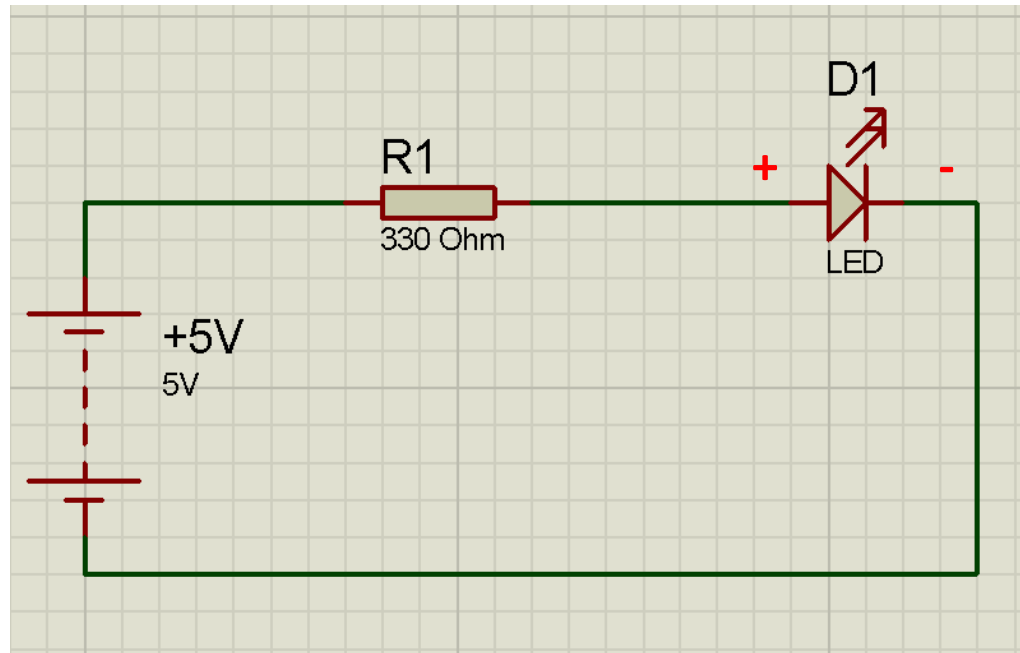


# Button Devresi

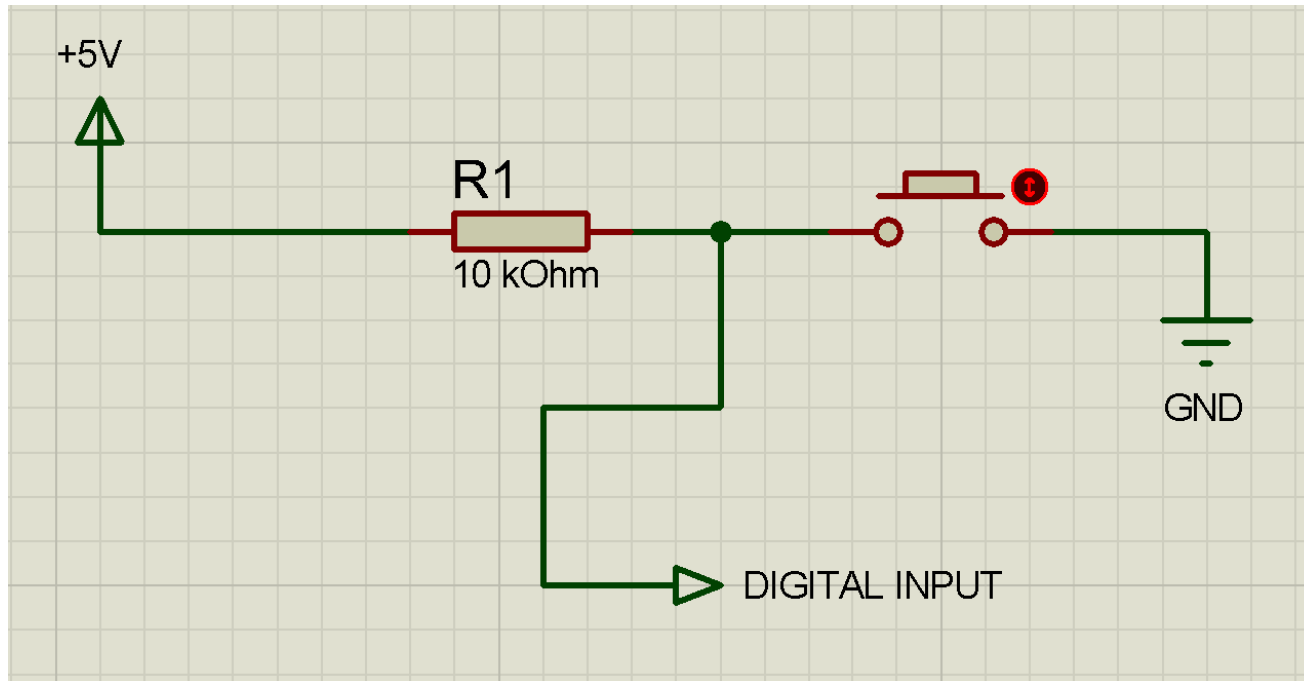




# Capacitors

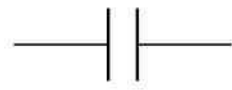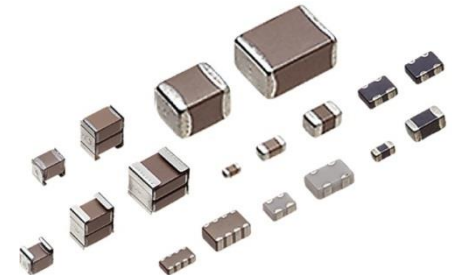


Normal (Ceramic)


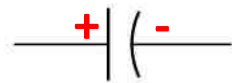


Electrolytic



# Diyot

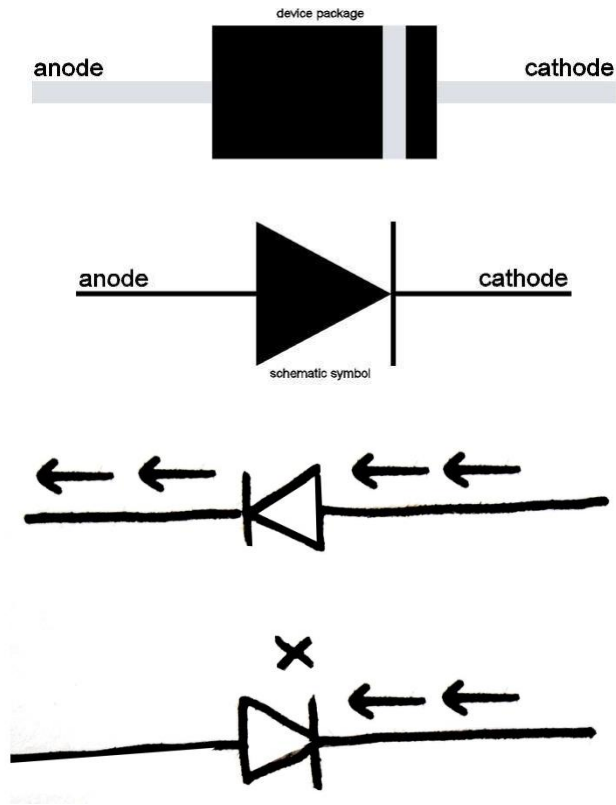

# Transistor

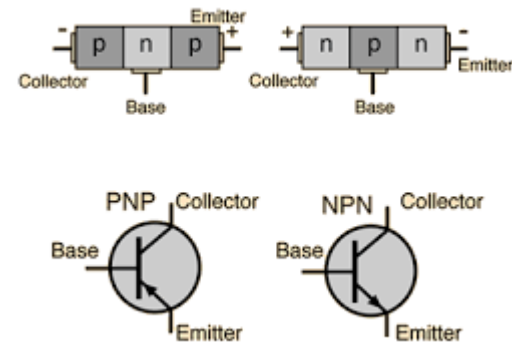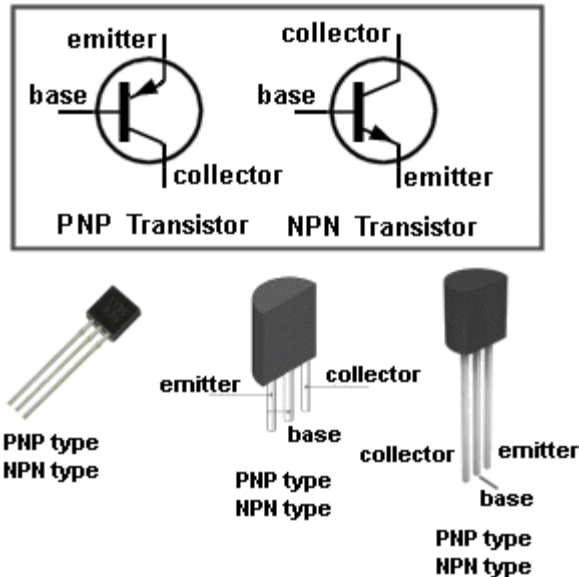


# MOSFET

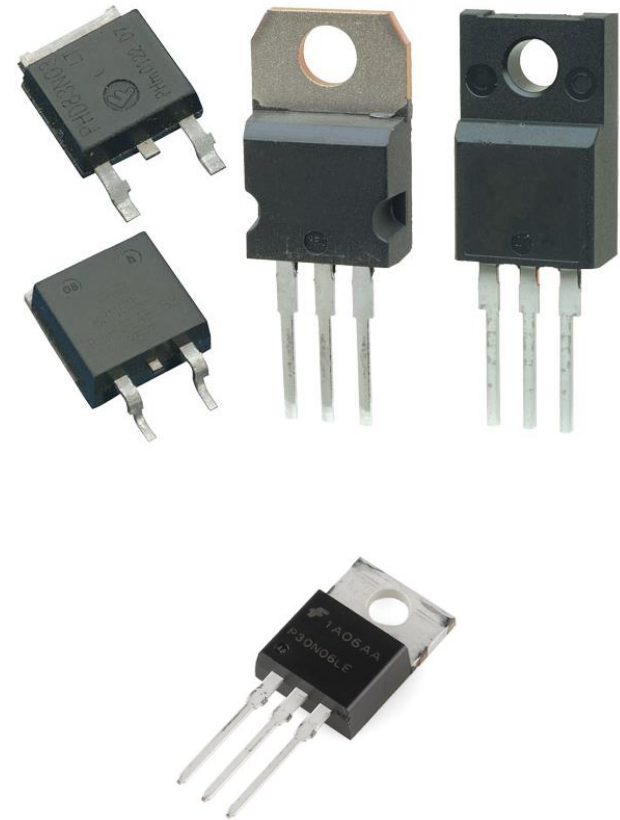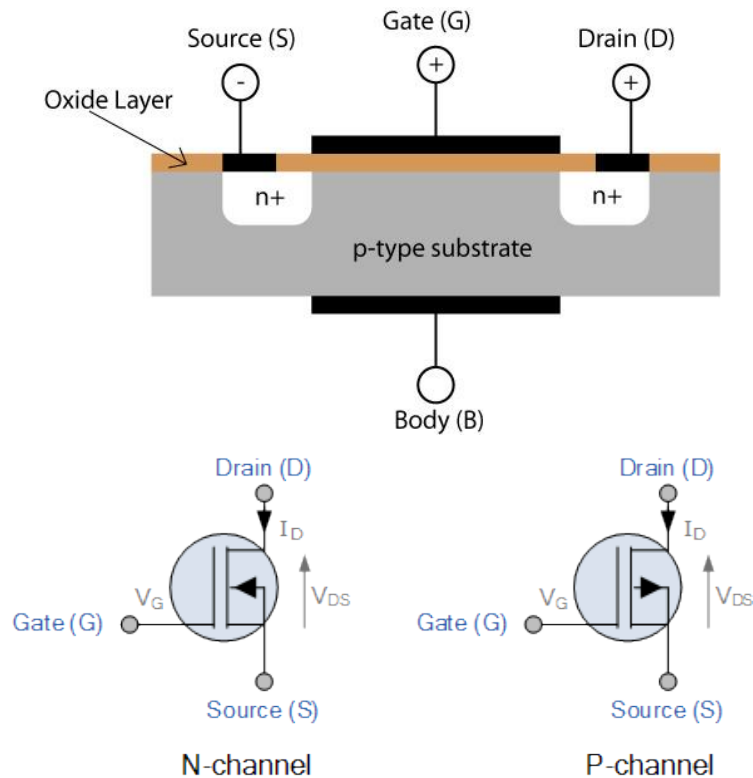

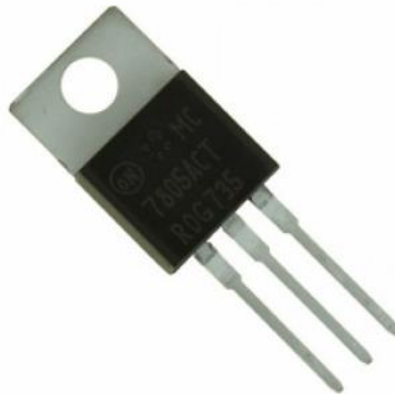
# LM78xx – Fixed Regulators

- Maximum current: 1A


- LM 7805
- LM 7808
- LM 7809
- LM 7812
- LM 7815



LM7805 PINOUT DIAGRAM

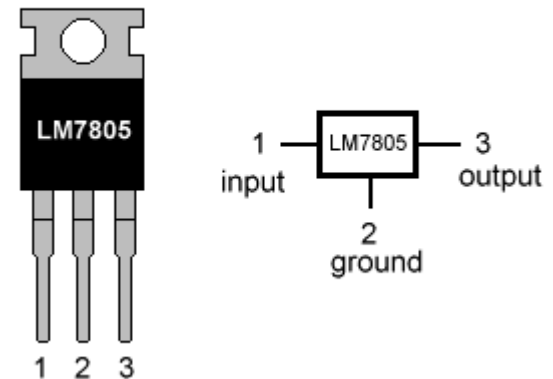


# Adjustable Regulators

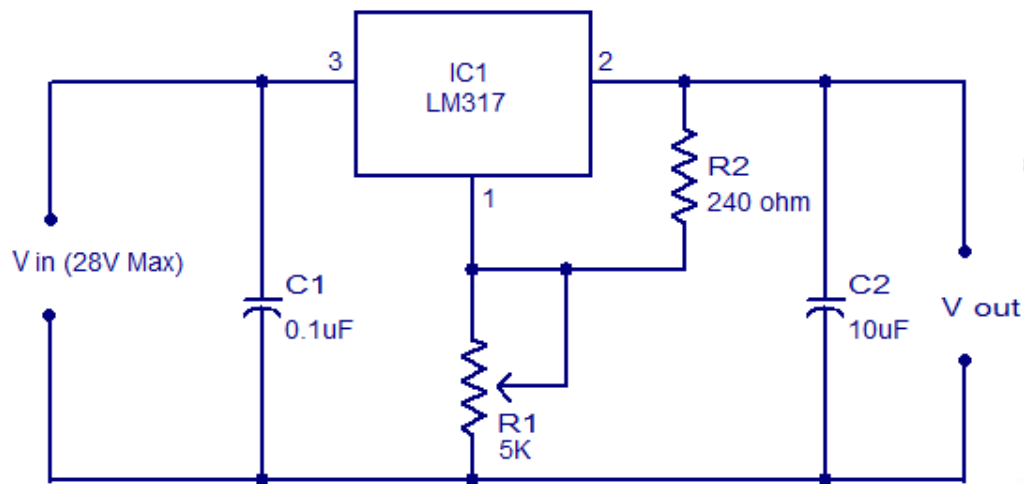

Typical adjustable regulator using LM317

[www.circuitstoday.com](http://www.circuitstoday.com)

LM317  
Pin Arrangement

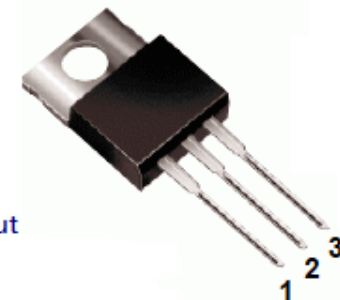

1. Adjust
2. Vout
3. Vin



Heatsink is connected to pin 2

$$V_{out} = 1.25V (1 + (R2/R1)) + (I_{adj} \times R2)$$

- Maximum current: 1,5A\*

\*LM317T datasheet'indeki verilere göre





# Adjustable Regulators

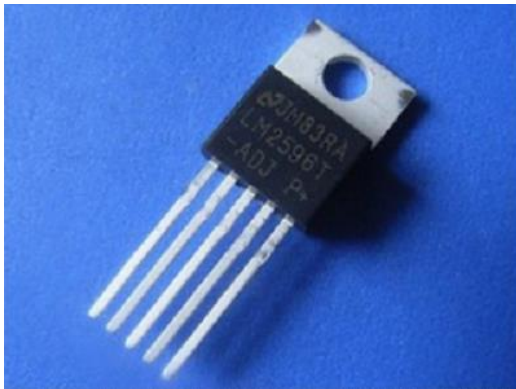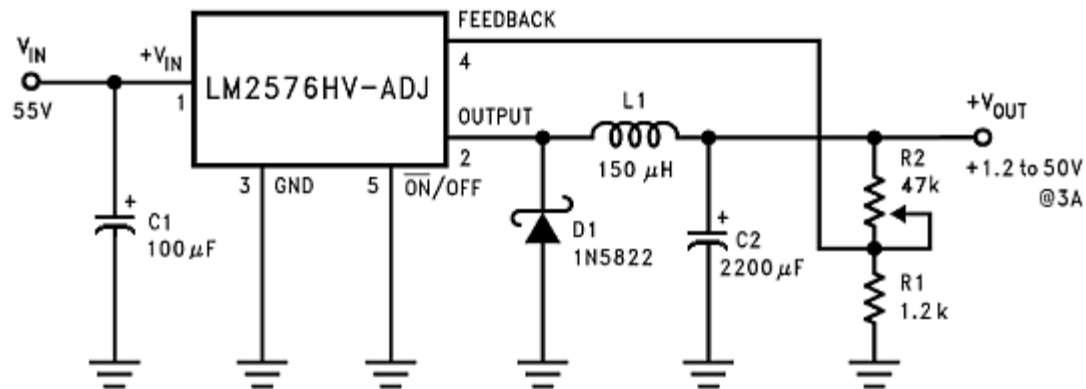

- Maximum current: 3A



# H-Bridge Motor Drivers

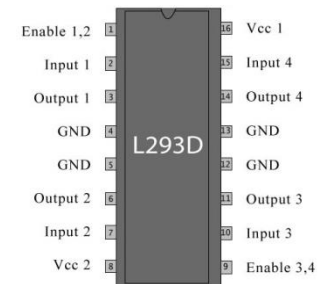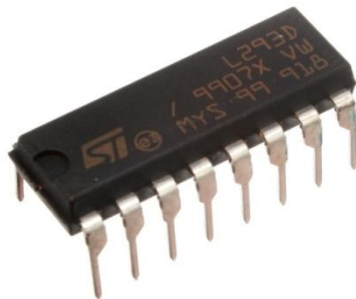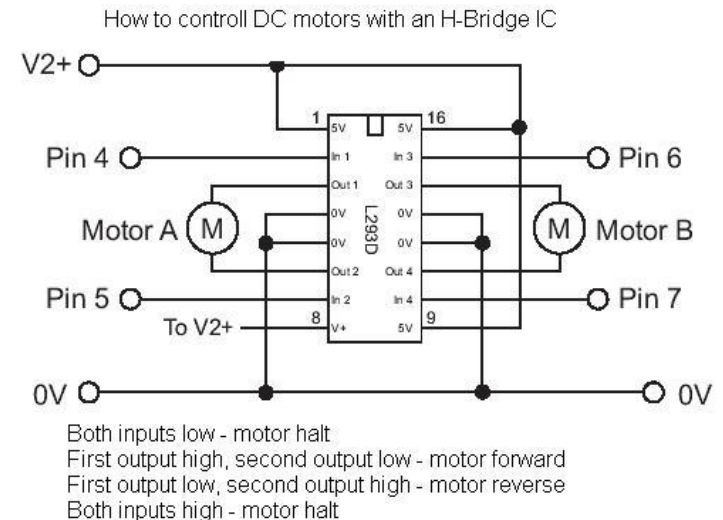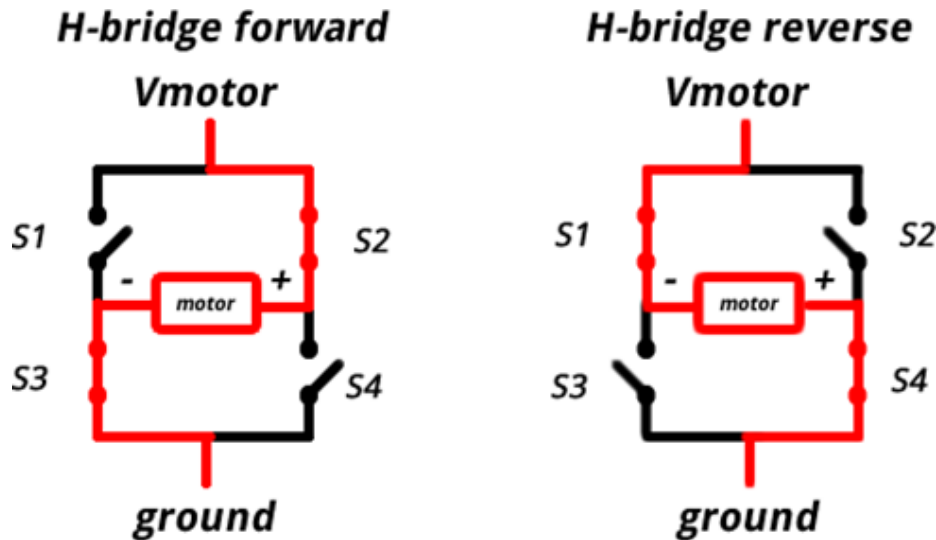



# Crystal Oscillator



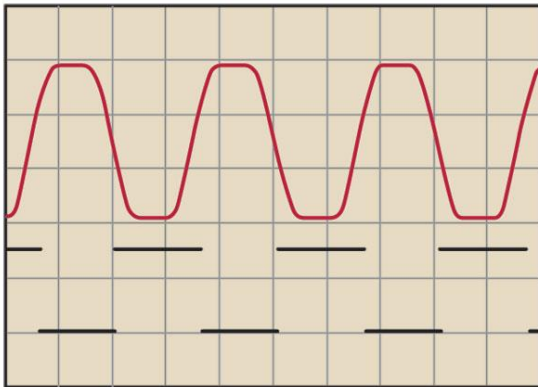


Fig 2. An oscilloscope photo shows the circuit's 32.768-kHz signals (at 10  $\mu\text{s}/\text{cm}$ ): the oscillator's output at 1 V/cm (top) and the buffer's output at 2 V/cm (bottom).


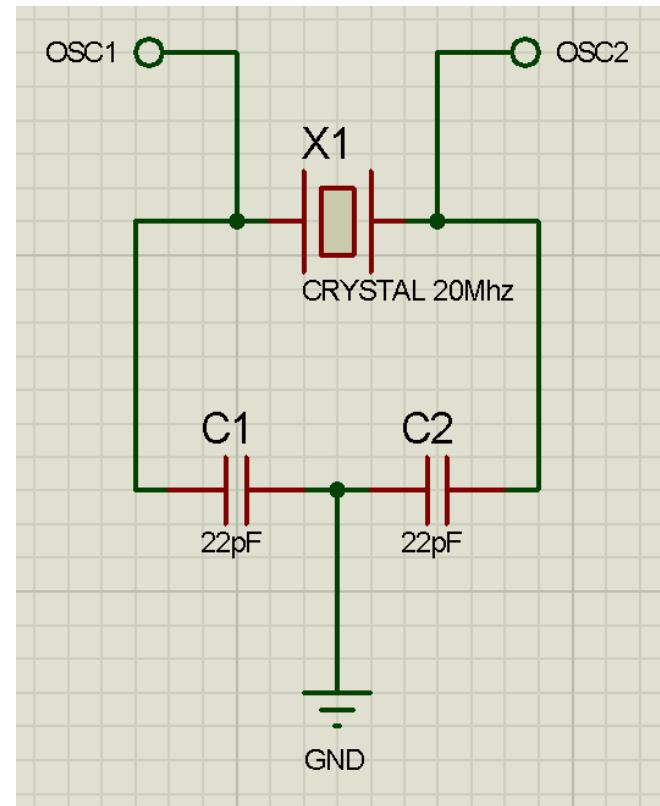


# Elektrik - Elektronik

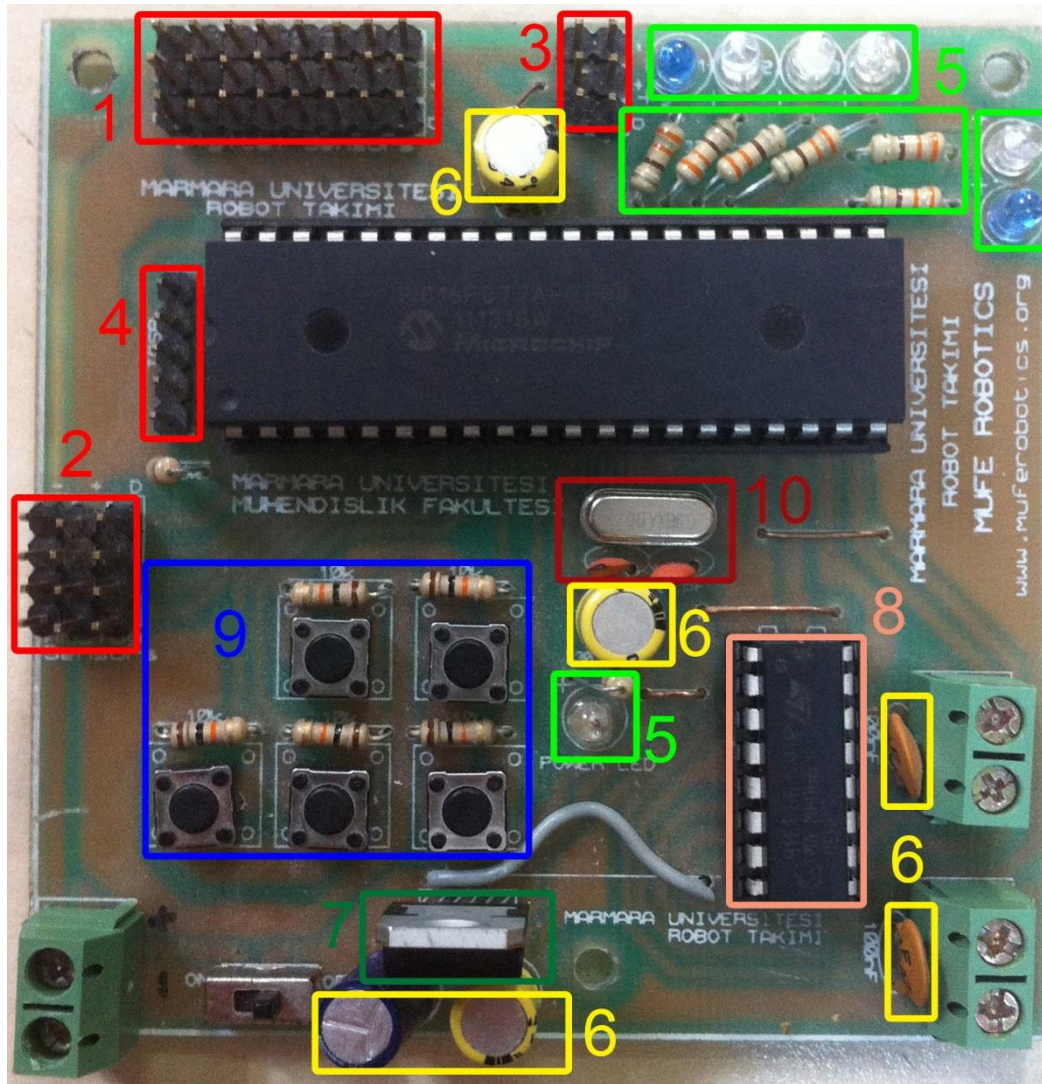

- 1- Digital I/O PINS PORT B
- 2- Analog I/O PINS PORT A
- 3- Digital I/O PINS PORT D
- 4- ICSP Program PINS
- 5- LED Devreleri
- 6- Capacitors (Ceramic / Electrolytic)
- 7- LM7805 – 5V Regulator
- 8- L293D – Motor Driver
- 9- Button Devreleri
- 10- Crystal Oscillator Devresi

# Elektrik - Elektronik

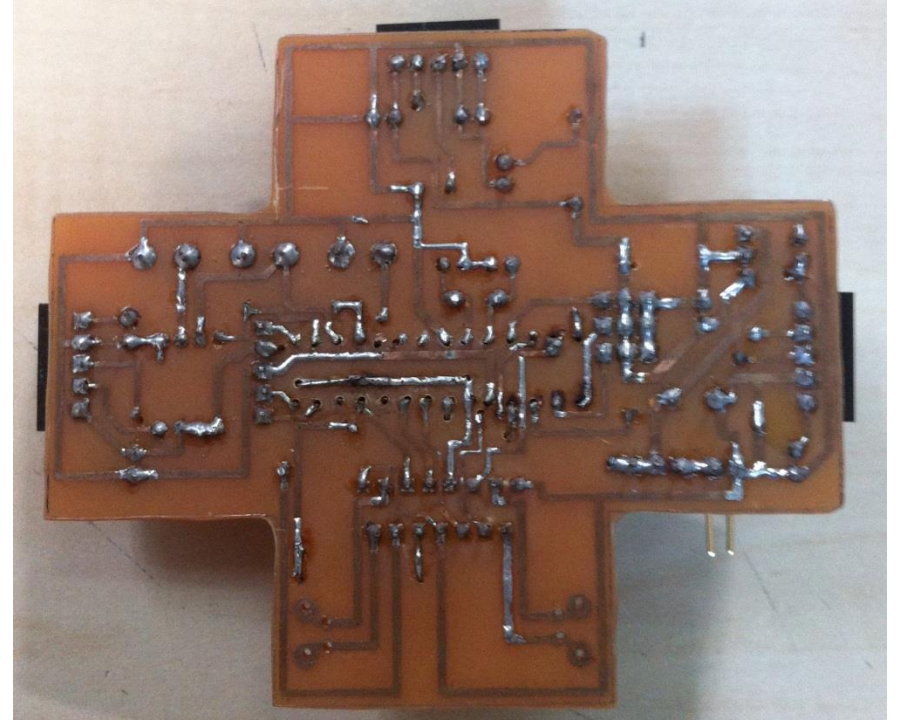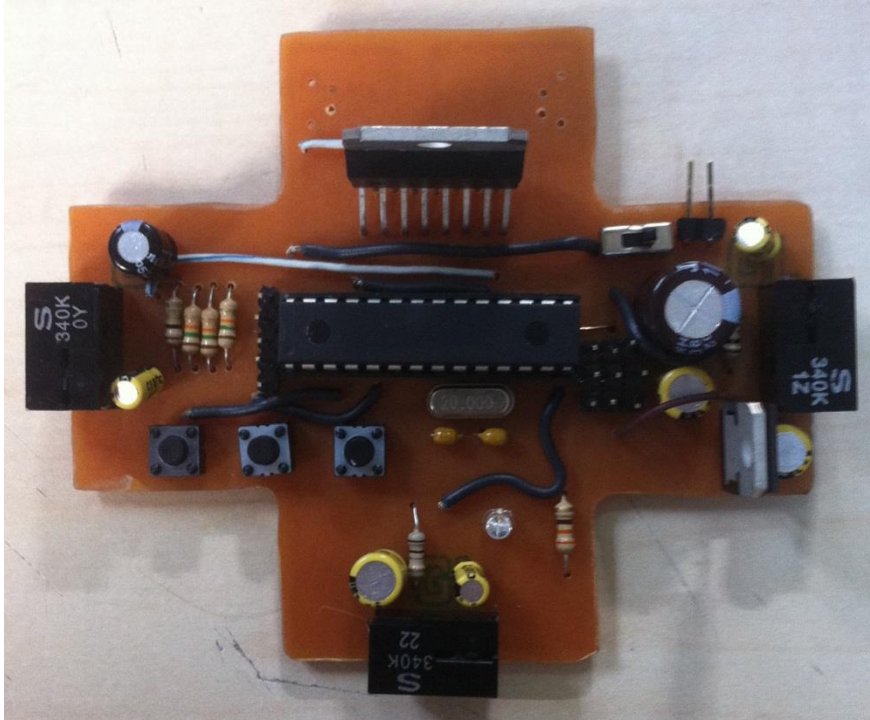


35mm

21mm



26mm

38mm

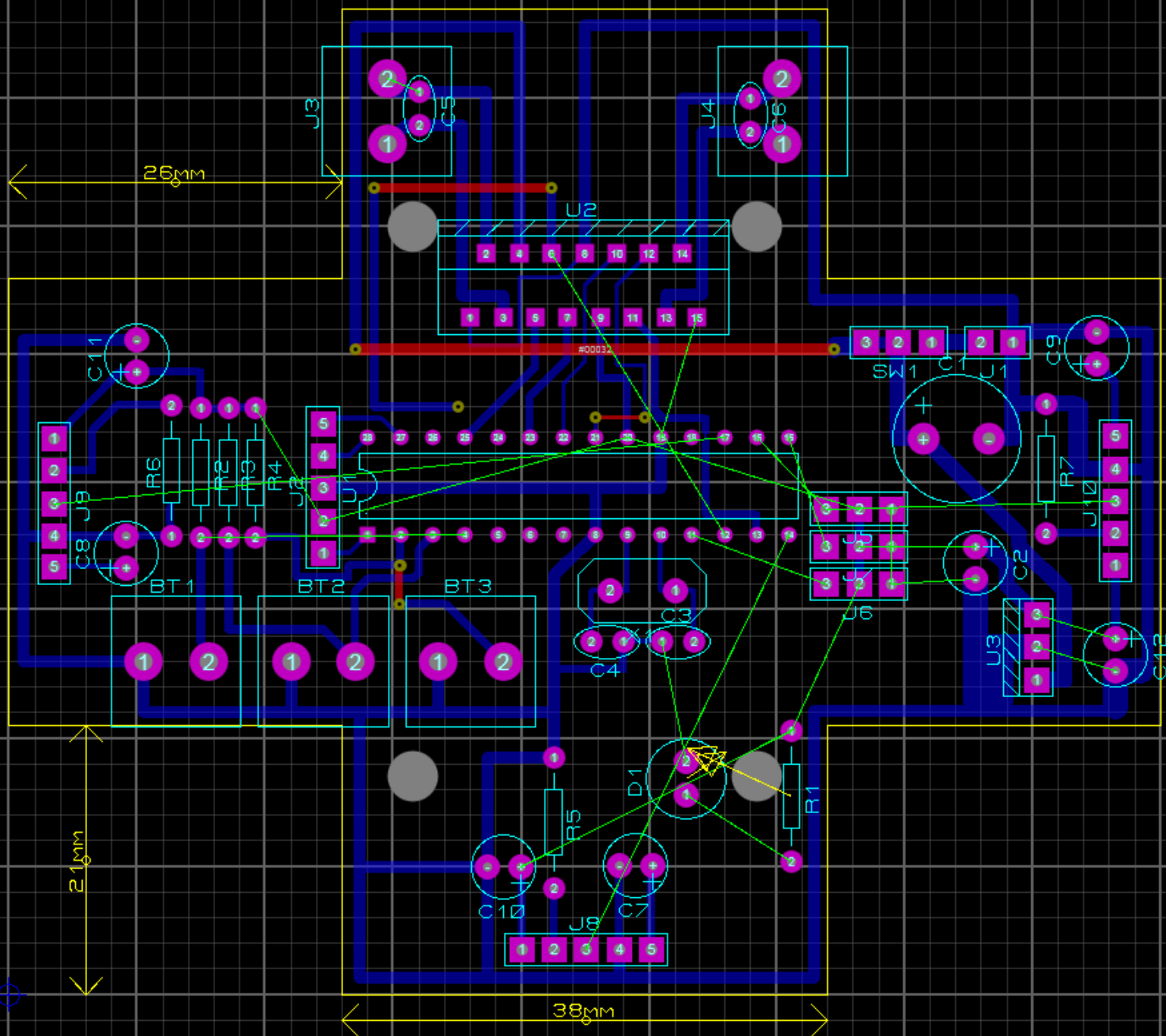



# Elektrik - Elektronik

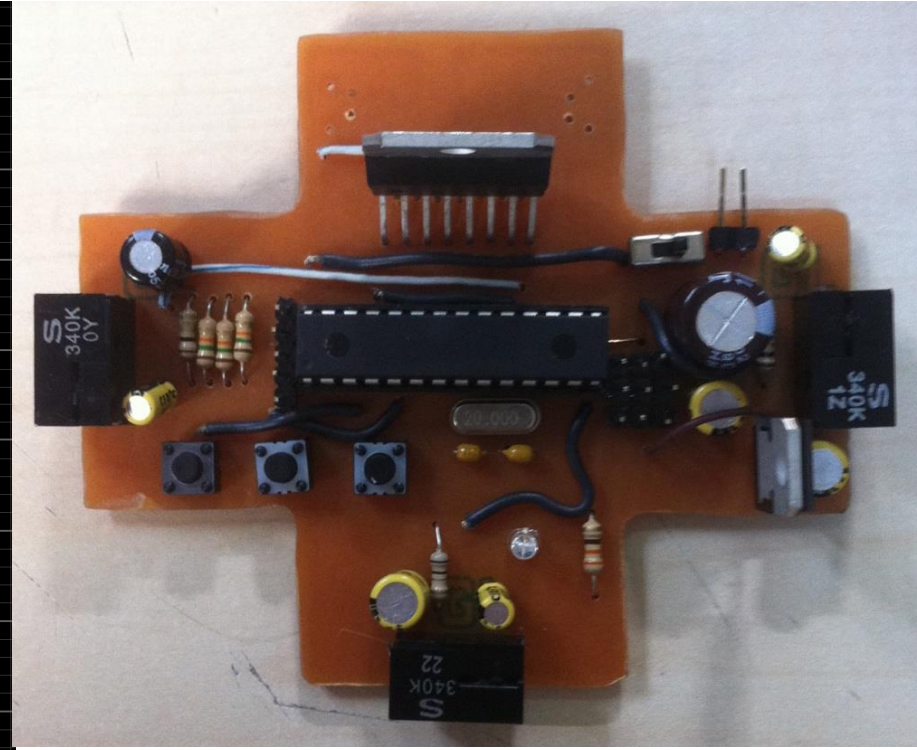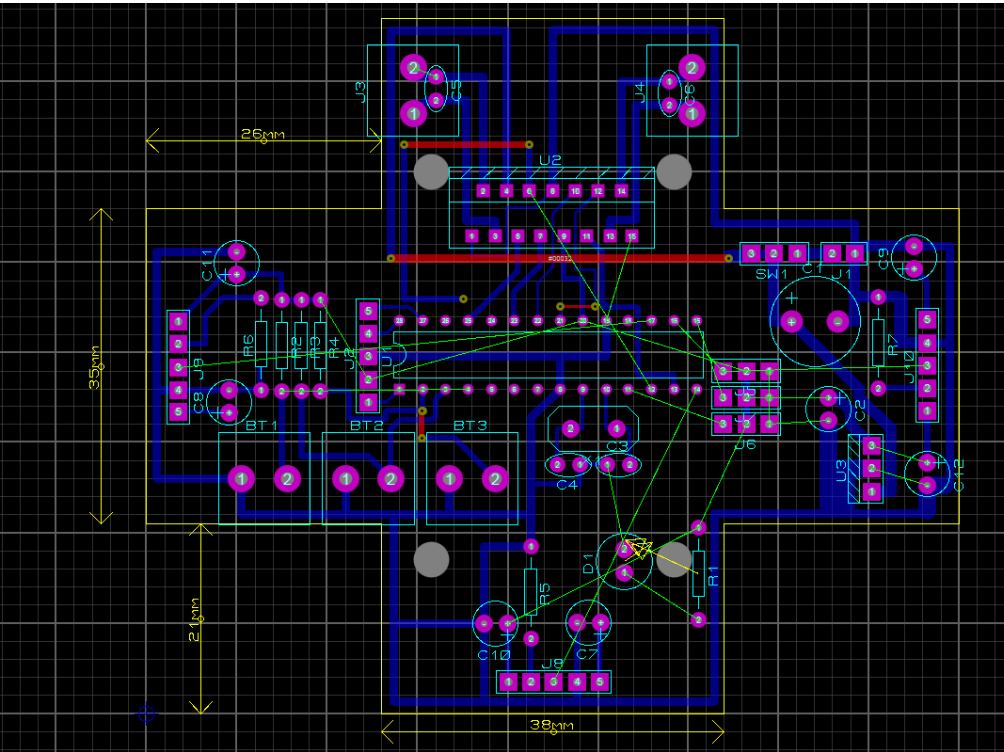


**Sorularınız?**

# Elektrik – Elektronik Giriş


## PCB Kart Basımı

# PCB Kart Basımı

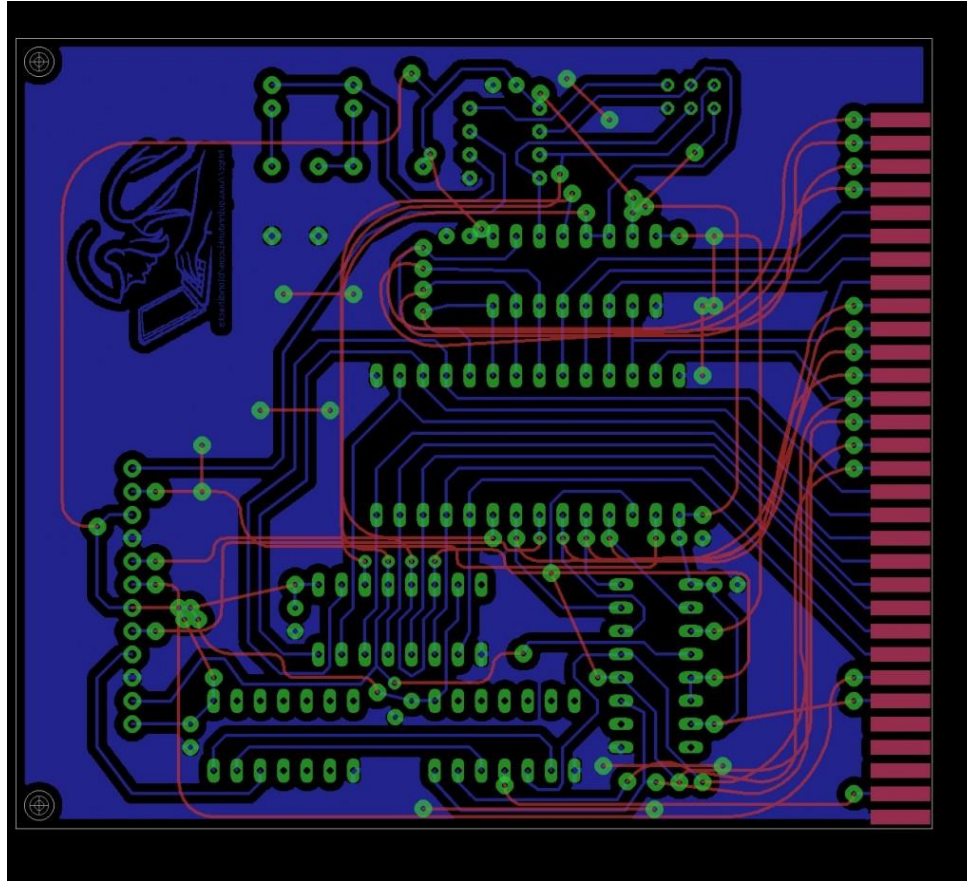




# PCB Kart Basımı

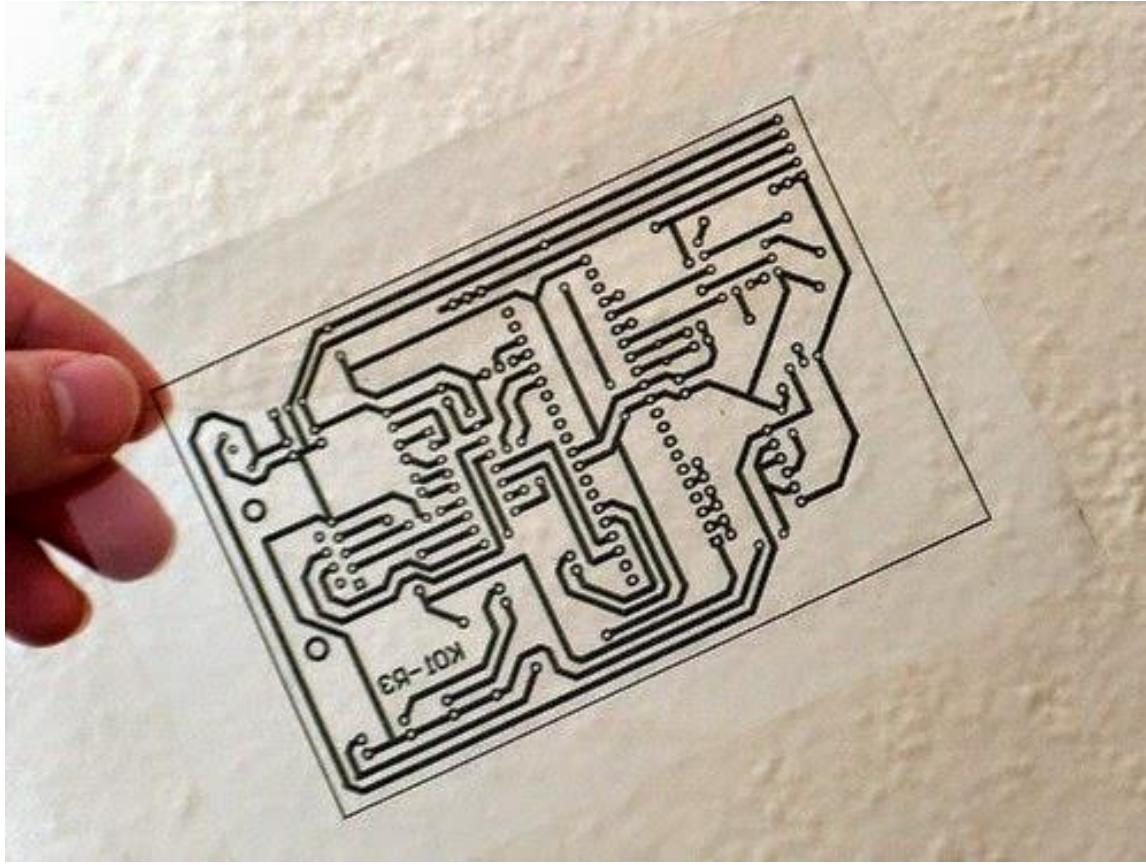

# PCB Kart Basımı



# PCB Kart Basımı

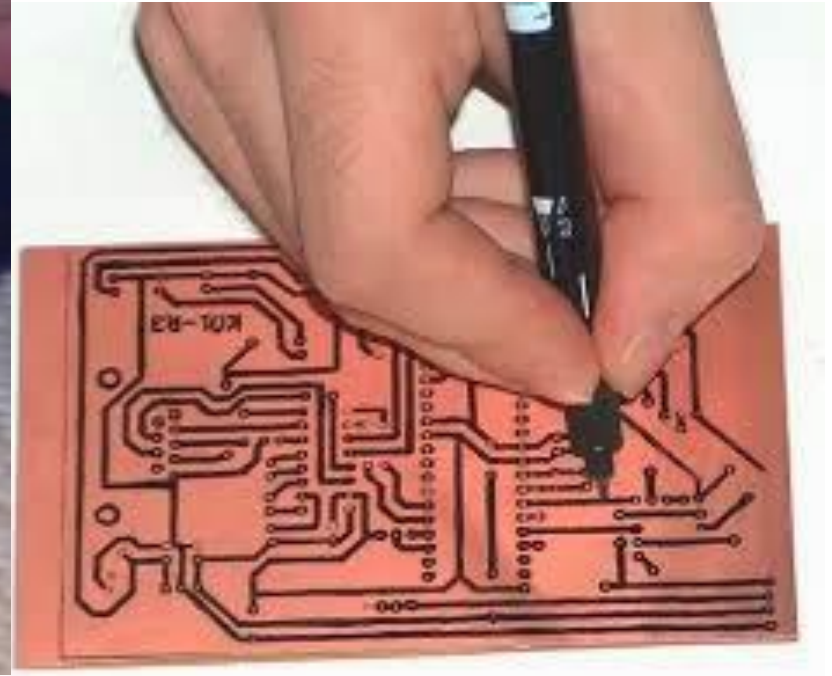




## Elektrik - Elektronik




# PCB Kart Basımı

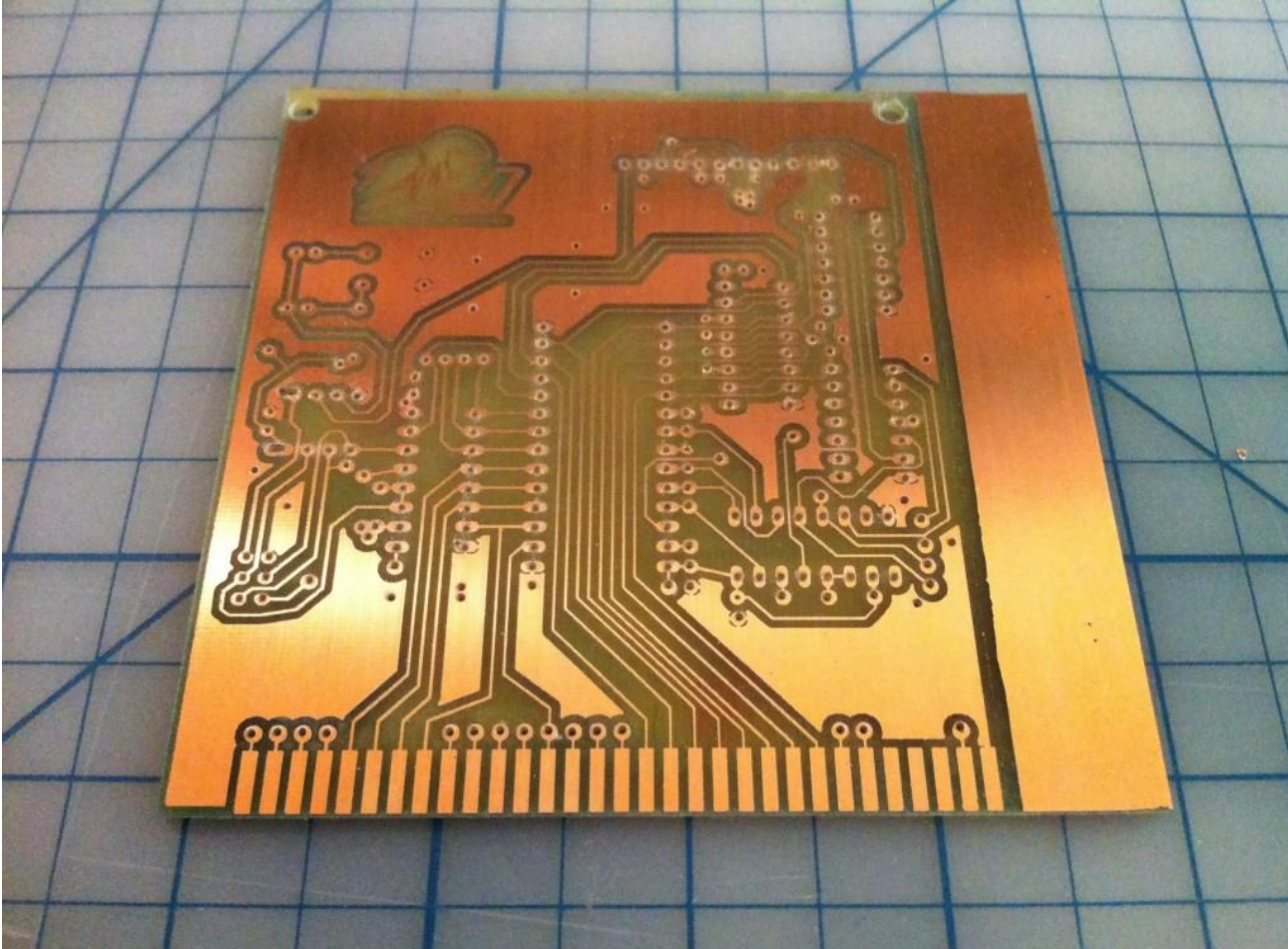






# PCB Kart Basımı

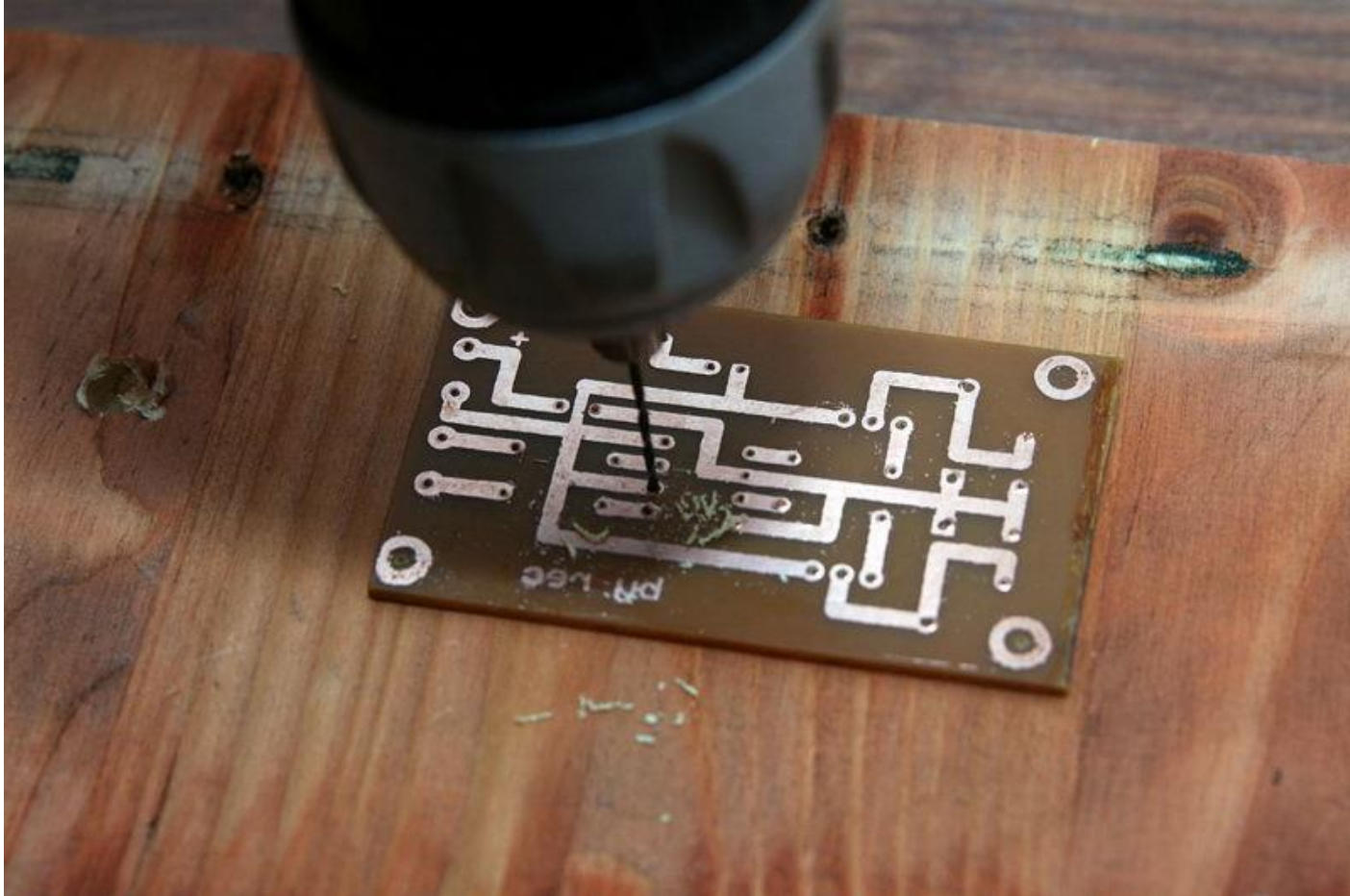

# PCB Kart Basımı


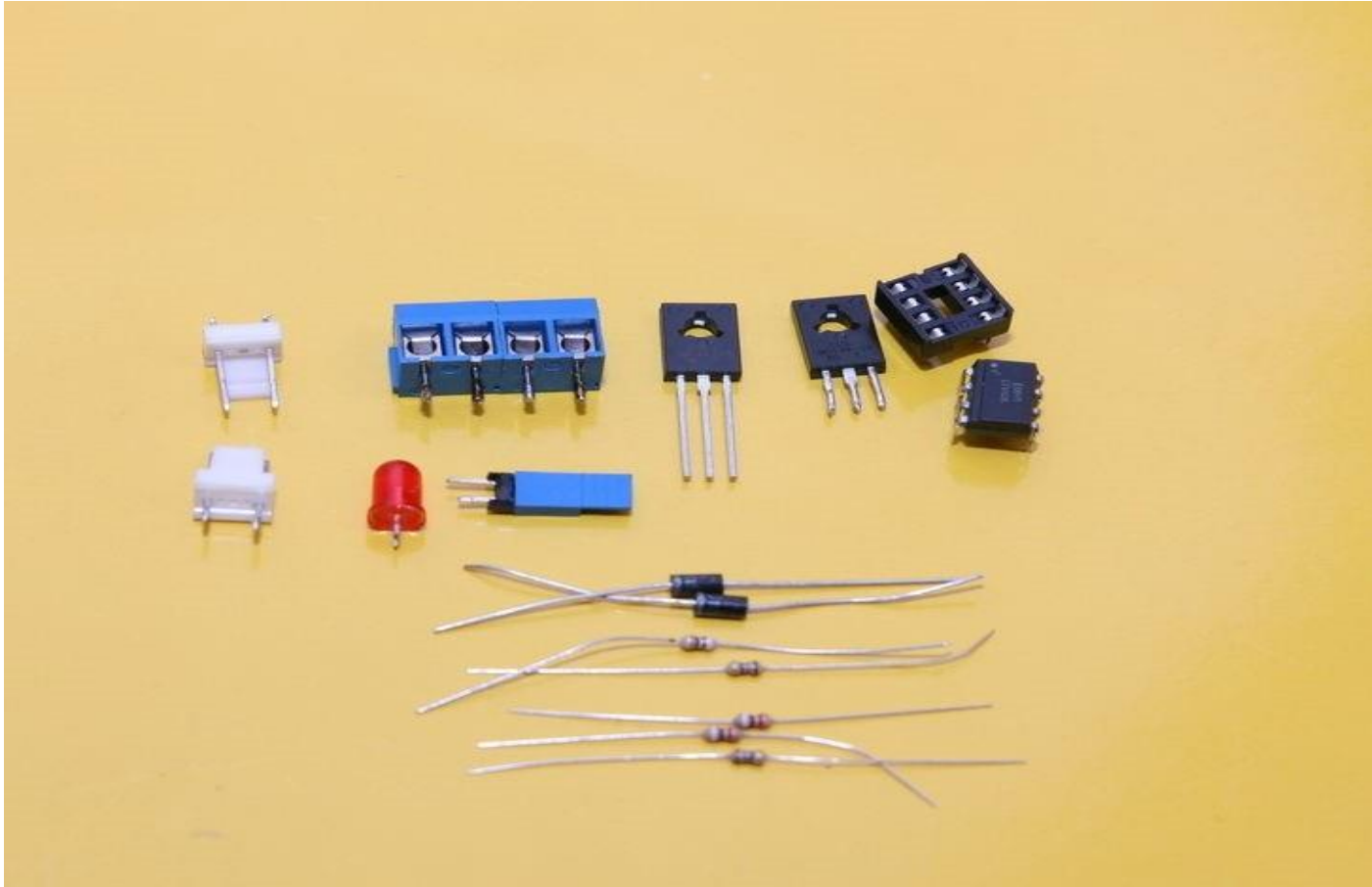


# PCB Kart Basımı

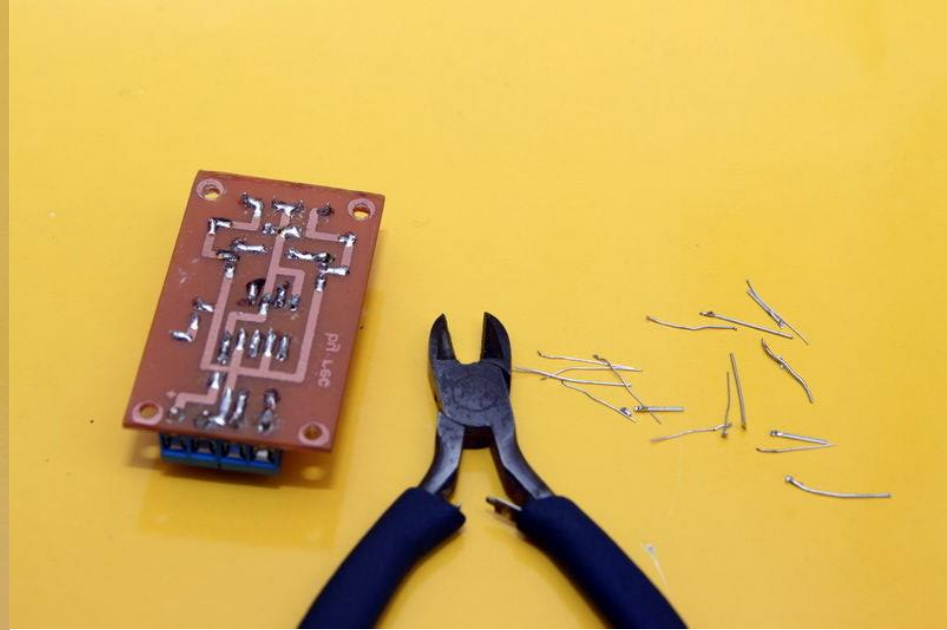
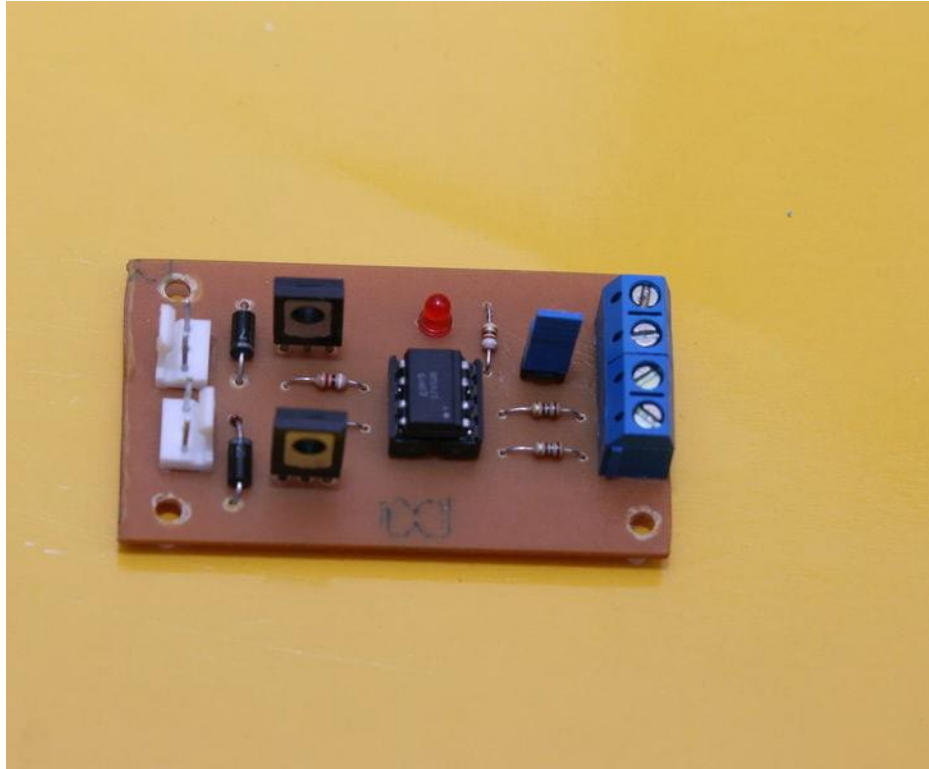




# Elektrik - Elektronik

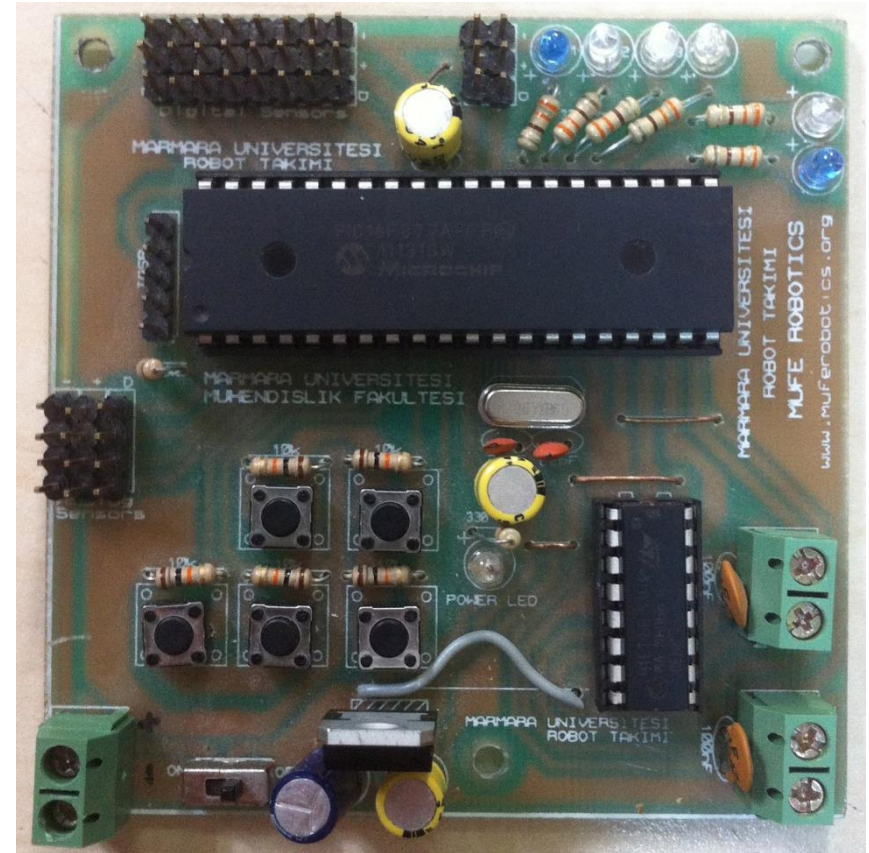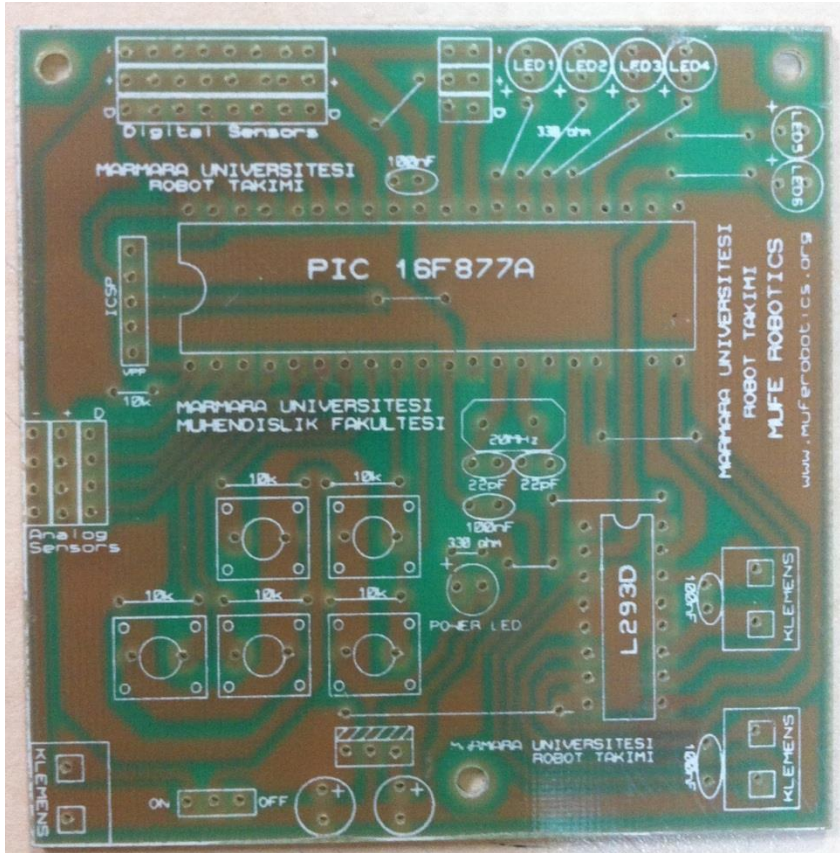


# Elektrik - Elektronik

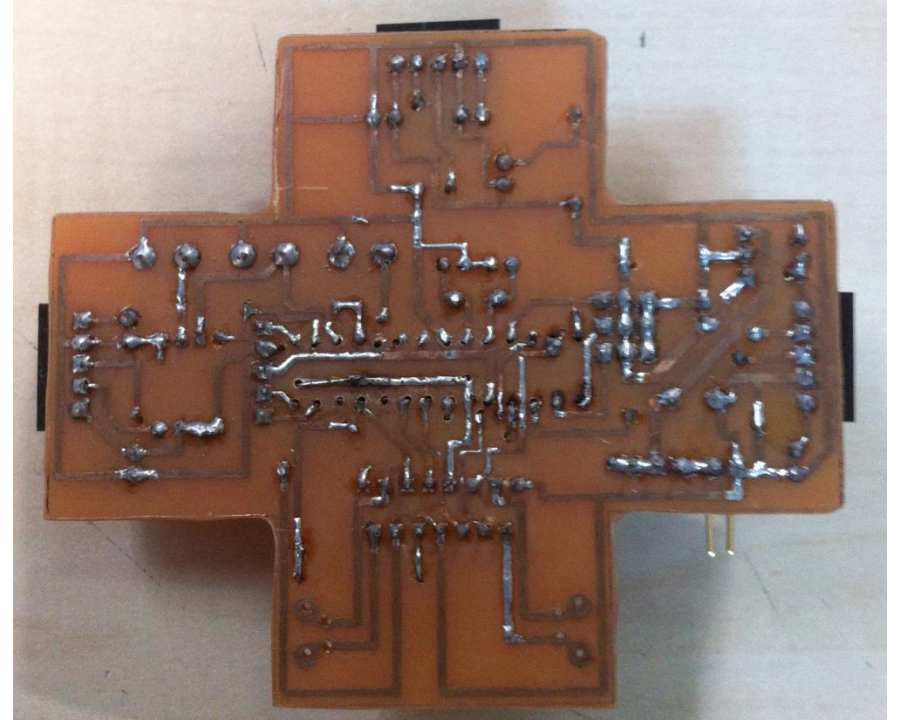
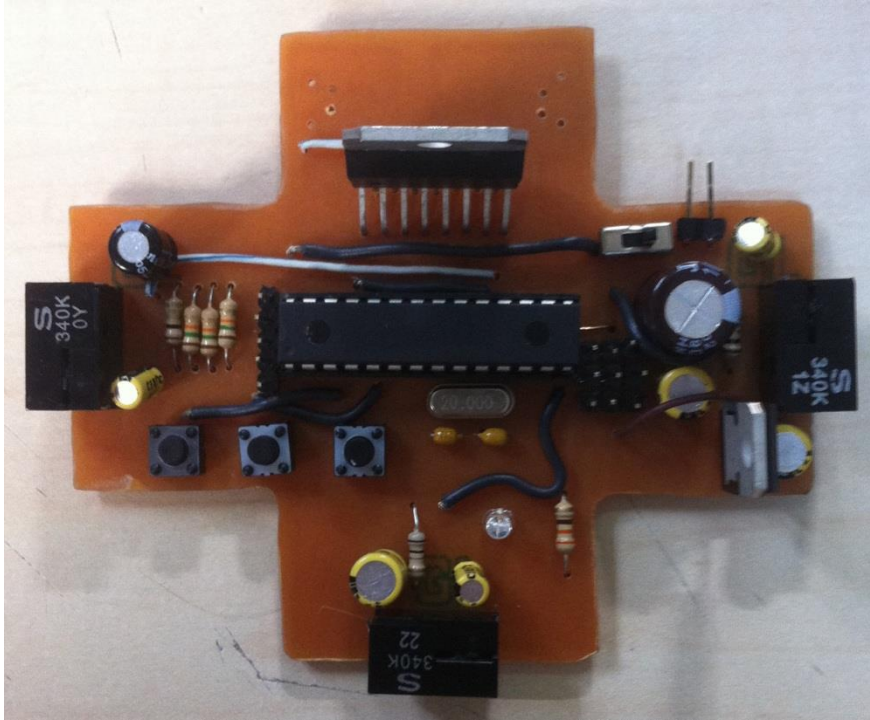



**Sorularınız?**

# Elektrik - Elektronik

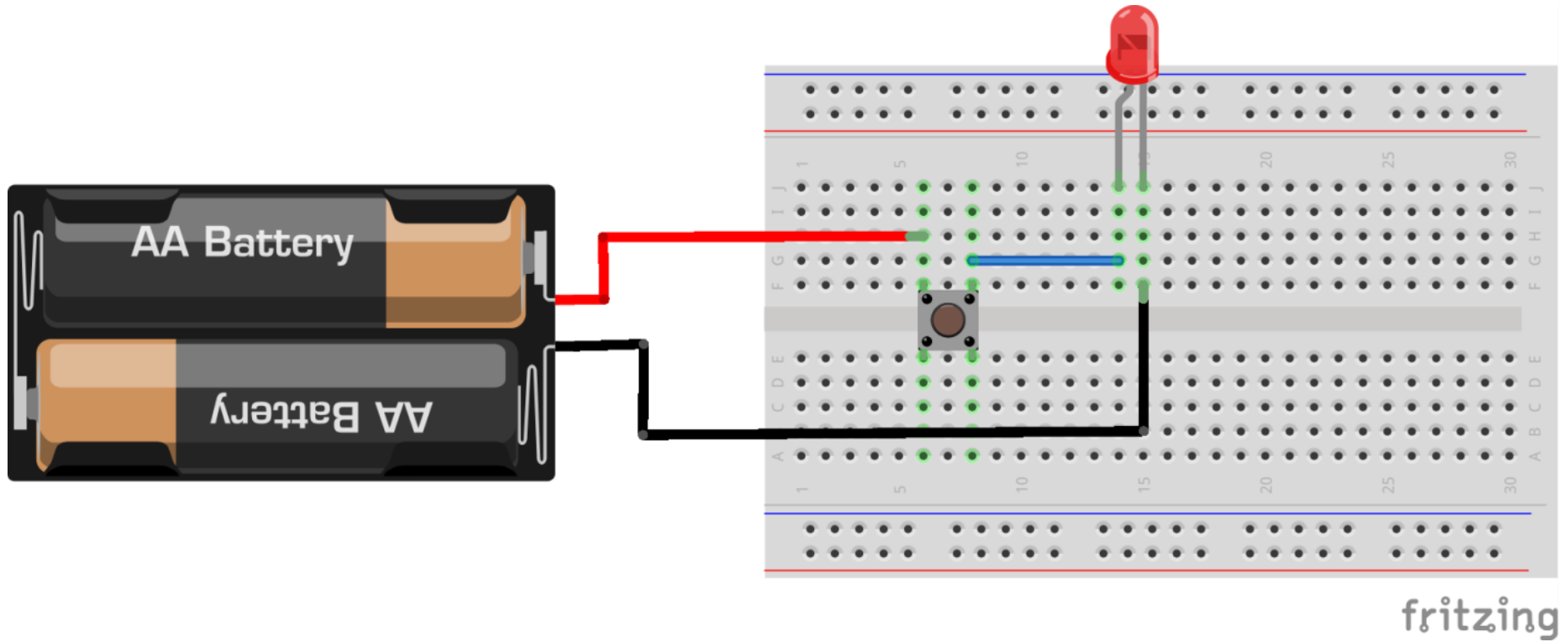



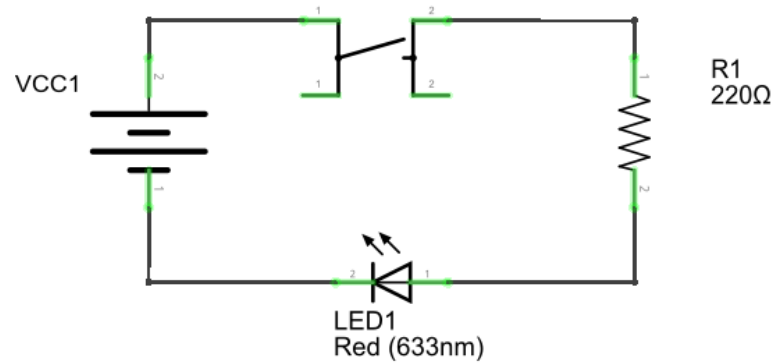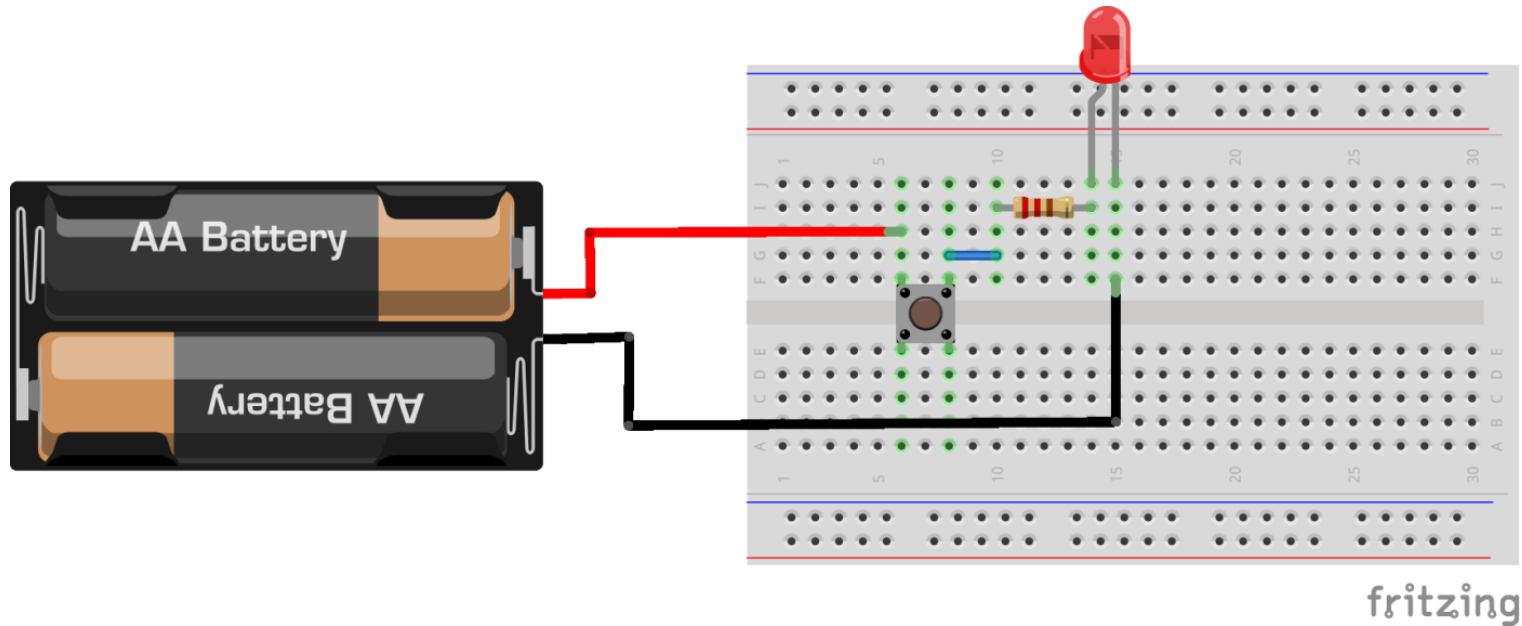

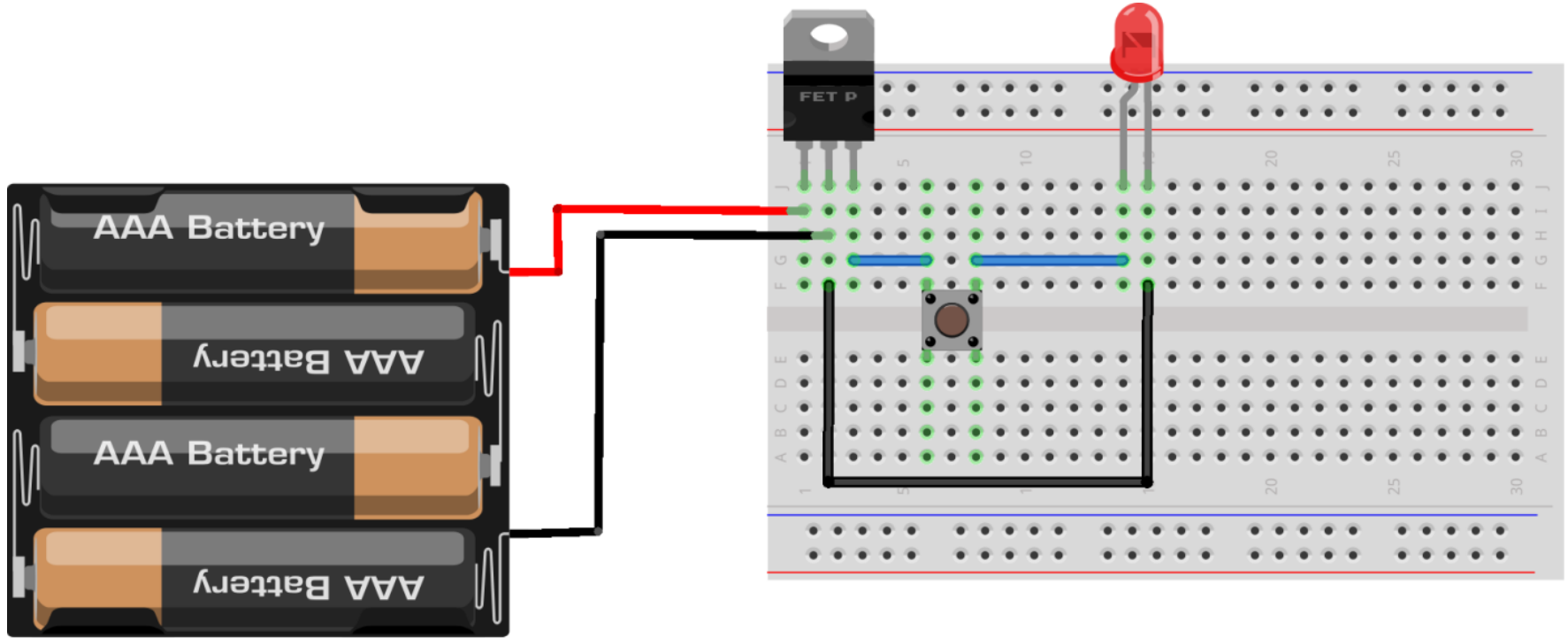

fritzing